

EL 6673 Resonant Power Converters Mini Project

Class D Voltage-source Half-bridge Inverter

Name: Lixue Zhang ID: N18499870 Date: 07/18/2016

I choose Class D FULL-BRIDGE PARALLEL-RESONANT INVERTER and the data from Problem 7.5.


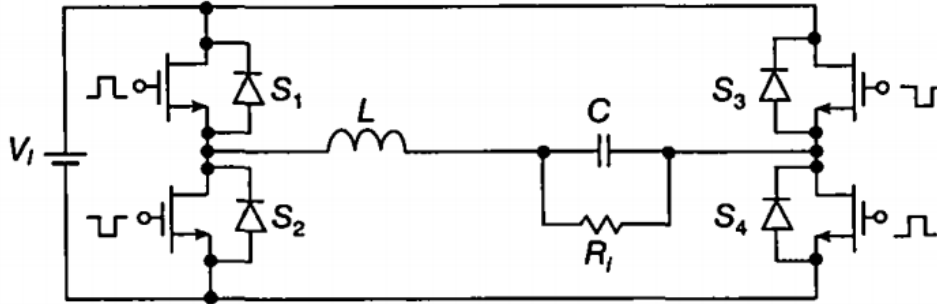



FIGURE 7.29 Circuit of the Class D full-bridge parallel resonant inverter.

Data: $V_I = 200$ V, $P_{R_i} = 75$ W, $f = 100$ kHz, $\eta_I = 92\%$. $Q = 2.5; 5; 8; 10$.

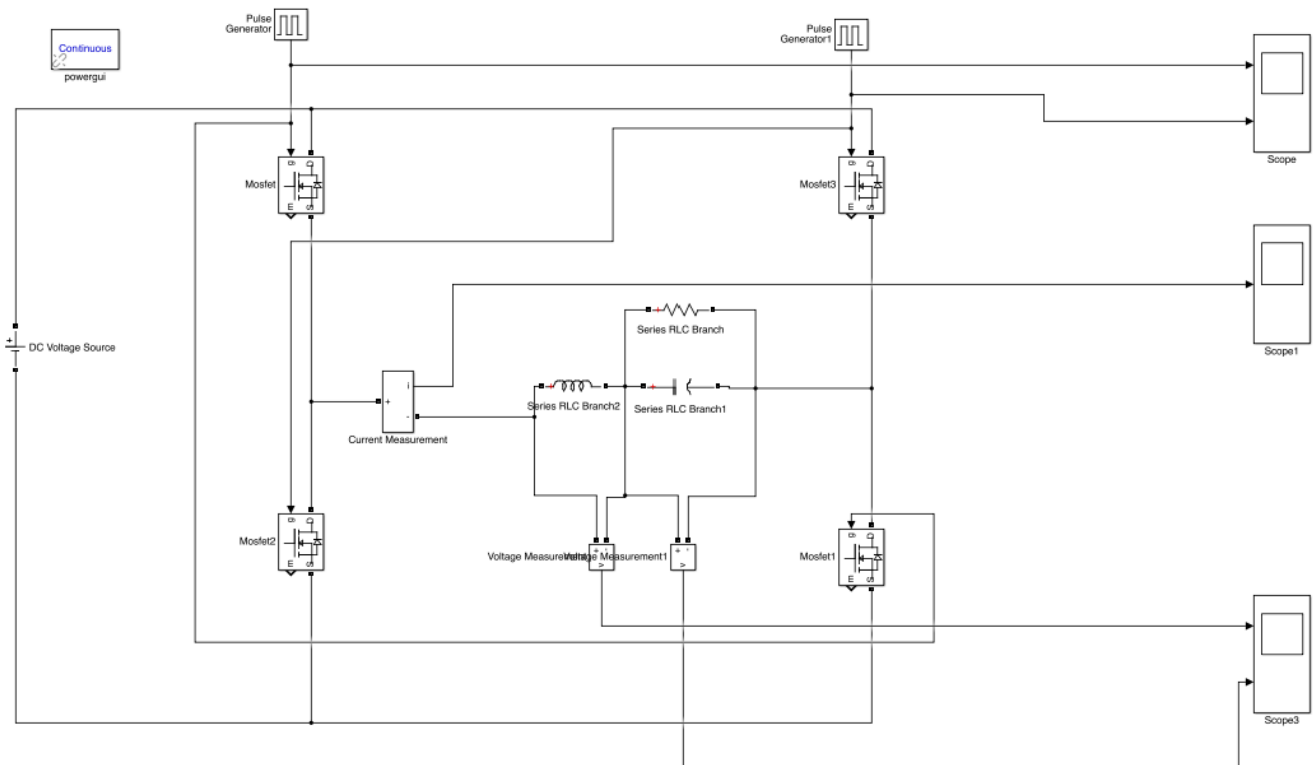1. Perform time-domain simulations of your selected inverter as follow:



The pulse waveform is:

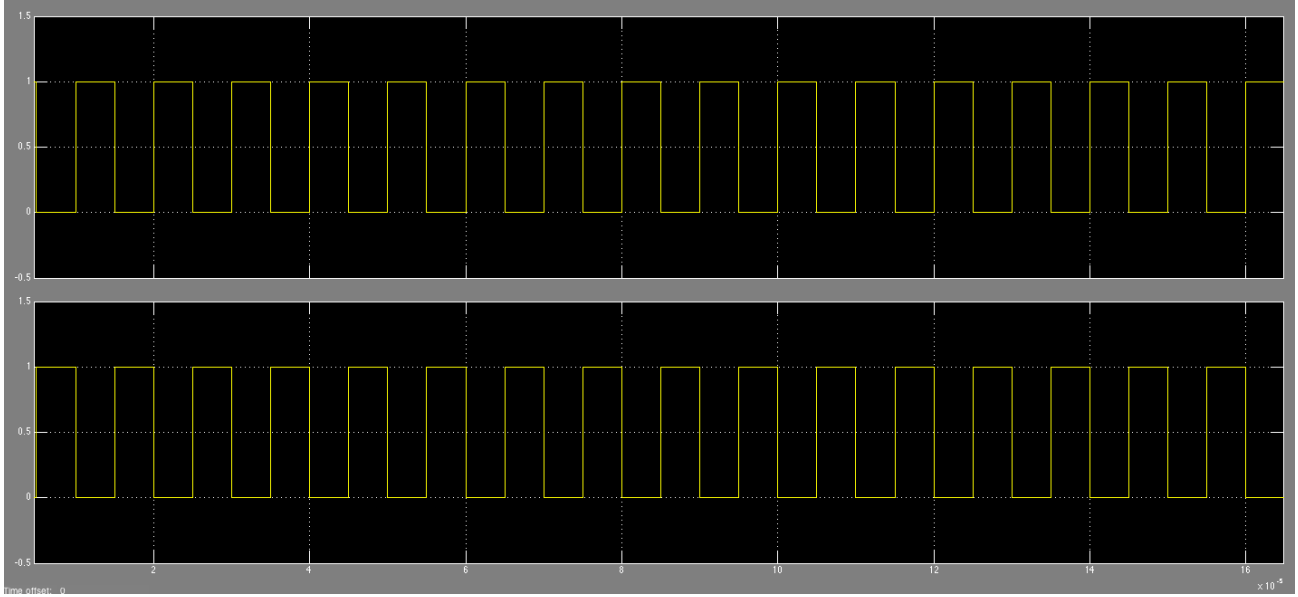

2. Show current and voltage waveforms in resonant components at various values of Q .
 If $Q=2.5$, then according to Problem 7.5, the calculating process is shown below:
 The dc supply power is

$$P_I = \frac{P_o}{\eta_I} = \frac{75}{0.92} = 81.52 \text{ W}$$

and the dc supply current is

$$I_I = \frac{P_I}{V_I} = \frac{81.52}{200} = 407.6 \text{ mA}$$

Assuming that $f = f_r = 100 \text{ kHz}$ at full power, the corner frequency is

$$f_o = \frac{f}{\sqrt{1 - \frac{1}{Q_L^2}}} = \frac{100 \times 10^3}{\sqrt{1 - \frac{1}{2.5^2}}} = 109.1 \text{ kHz}$$

the ac load resistance of the inverter

$$R_i = \frac{8V_I^2 \eta_I^2}{\pi^2 P_{Ri} \left\{ \left[1 - \left(\frac{\omega}{\omega_o} \right)^2 \right]^2 + \left[\frac{1}{Q_L} \left(\frac{\omega}{\omega_o} \right) \right]^2 \right\}} = \frac{8 \times 200^2 \times 0.92^2}{\pi^2 \times 75 \times \left\{ \left[1 - \left(\frac{100}{109.1} \right)^2 \right]^2 + \left[\frac{1}{2.5} \left(\frac{100}{109.1} \right) \right]^2 \right\}} = 2287.2 \Omega$$

the characteristic impedance is

$$Z_o = \frac{R_i}{Q_L} = \frac{2287.2}{2.5} = 914.9 \Omega$$

the elements of the resonant circuit are

$$L = \frac{Z_o}{\omega_o} = \frac{914.9}{2\pi \times 109.1 \times 10^3} = 1.335 \text{ mH}$$

and

$$C = \frac{1}{\omega_o Z_o} = \frac{1}{2\pi \times 109.1 \times 10^3 \times 914.9} = 1.59 \text{ nF}$$

the peak value of the switch current is

$$I_m = I_{SM} = \frac{4V_I \sqrt{Q_L^2 + 1}}{\pi Z_o} = \frac{4 \times 200 \times \sqrt{2.5^2 + 1}}{\pi \times 914.9} = 0.75 \text{ A}$$


the voltage stresses of the resonant components are

$$V_{Cm} = \frac{4V_I Q_L}{\pi} = \frac{4 \times 200 \times 2.5}{\pi} = 636.6 \text{ V}$$


and

$$V_{Lm} = \frac{4V_I \sqrt{Q_L^2 + 1}}{\pi} = \frac{4 \times 200 \times \sqrt{2.5^2 + 1}}{\pi} = 685.6 \text{ V}$$

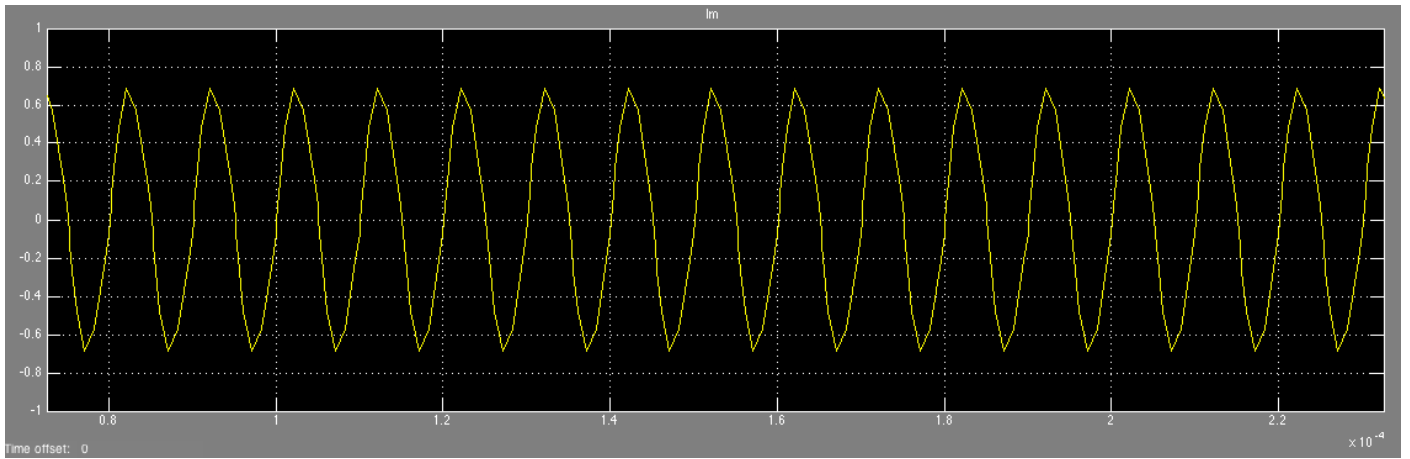a) Current and voltage waveform in resonant components I_m




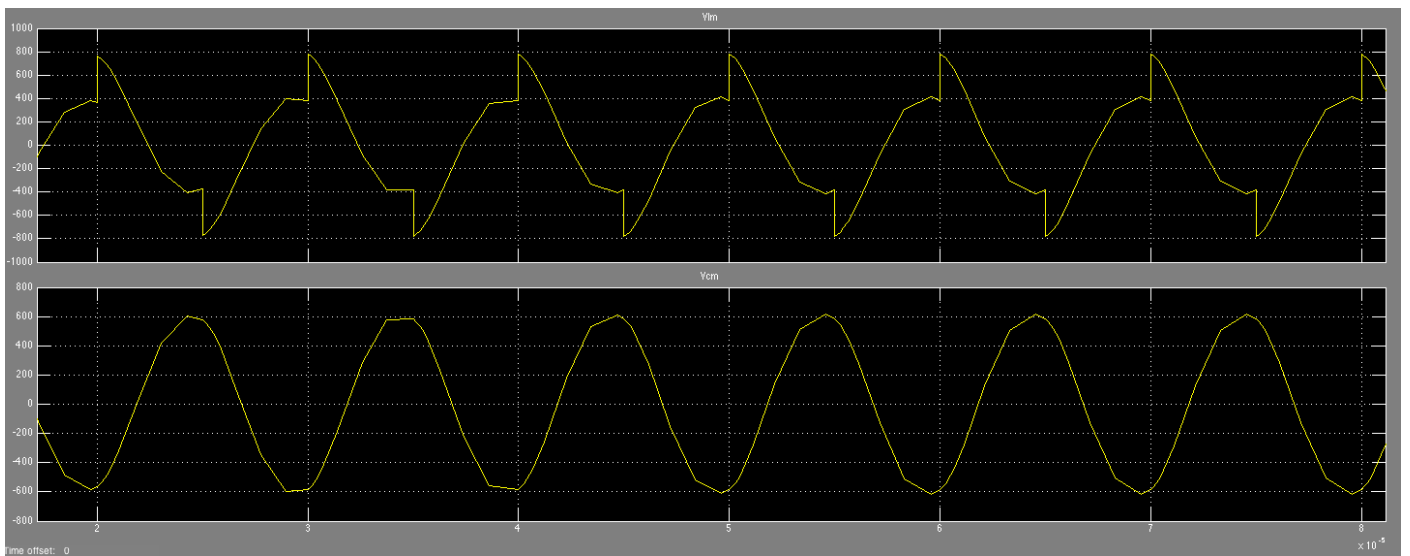b) Voltage waveform for resonant component V_{Lm} , V_{Cm}




If $Q=5$, then $f_o=102.06 \text{ kHz}$, $R_i=9147.9 \text{ } \Omega$, $L=2.85 \text{ mH}$, $C=0.8523 \text{ nF}$, $I_m=0.7097 \text{ A}$, $V_{Lm}=1273.24 \text{ V}$,
 $V_{Cm}=1298.45 \text{ V}$.

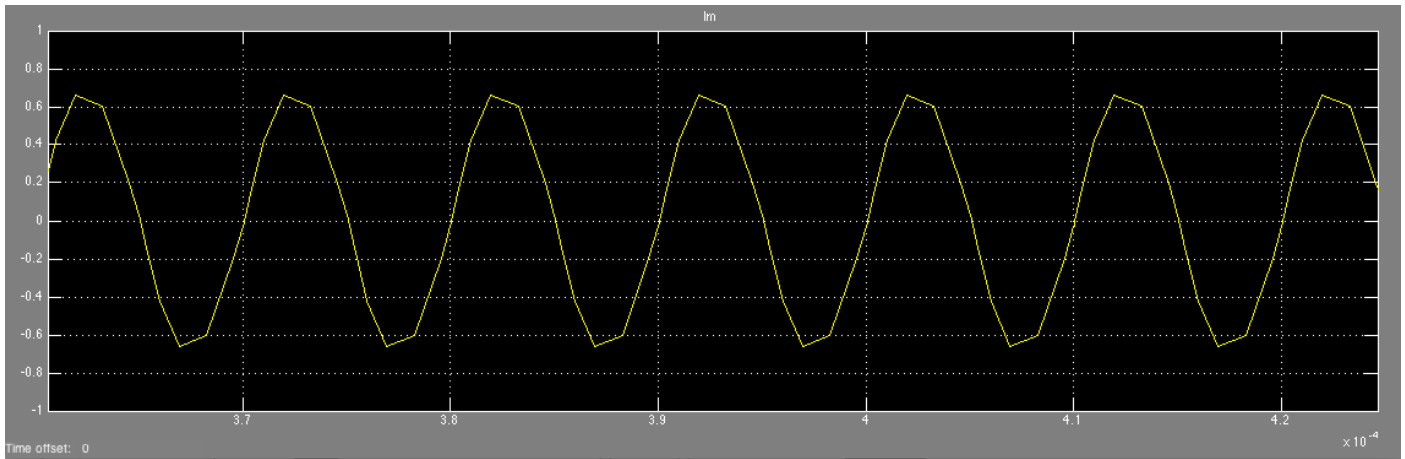c) Current and voltage waveform in resonant components I_m :




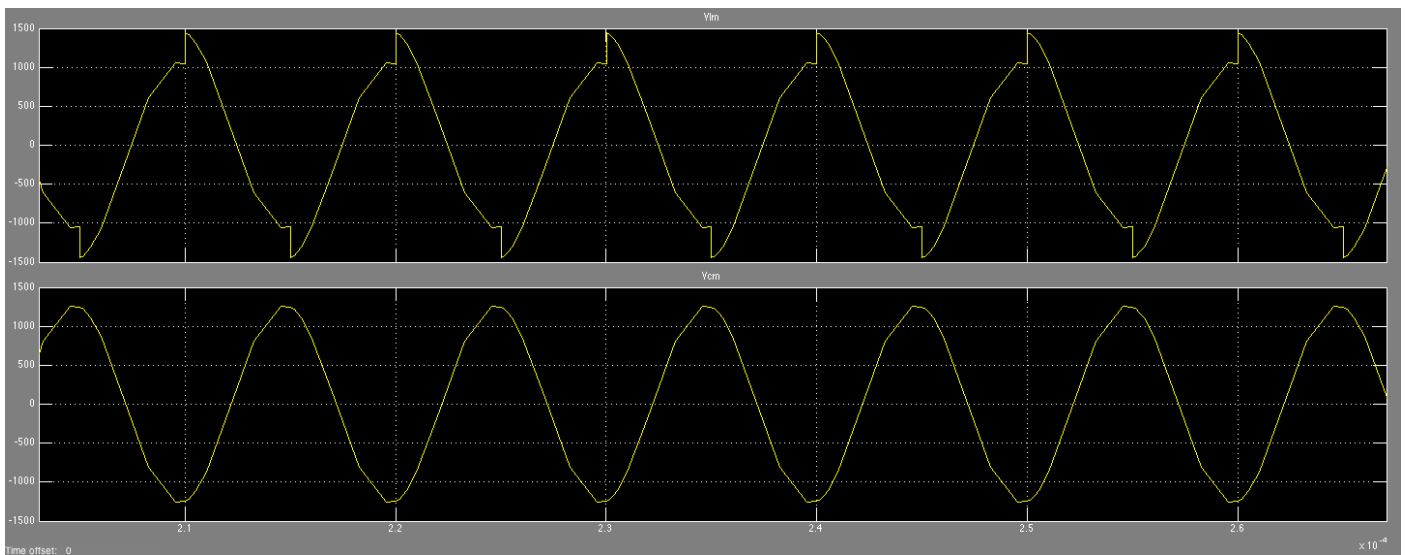d) Voltage waveform for resonant component V_{Lm} , V_{Cm}




If $Q=8$, then $f_o=100.79\text{kHz}$, $R_i=2.3418 \times 10^4 \Omega$, $L=4.622 \text{ mH}$, $C=0.5394 \text{ nF}$, $I_m=0.701 \text{ A}$, $V_{Lm}=2037.18 \text{ V}$, $V_{Cm}=2053.04 \text{ V}$.

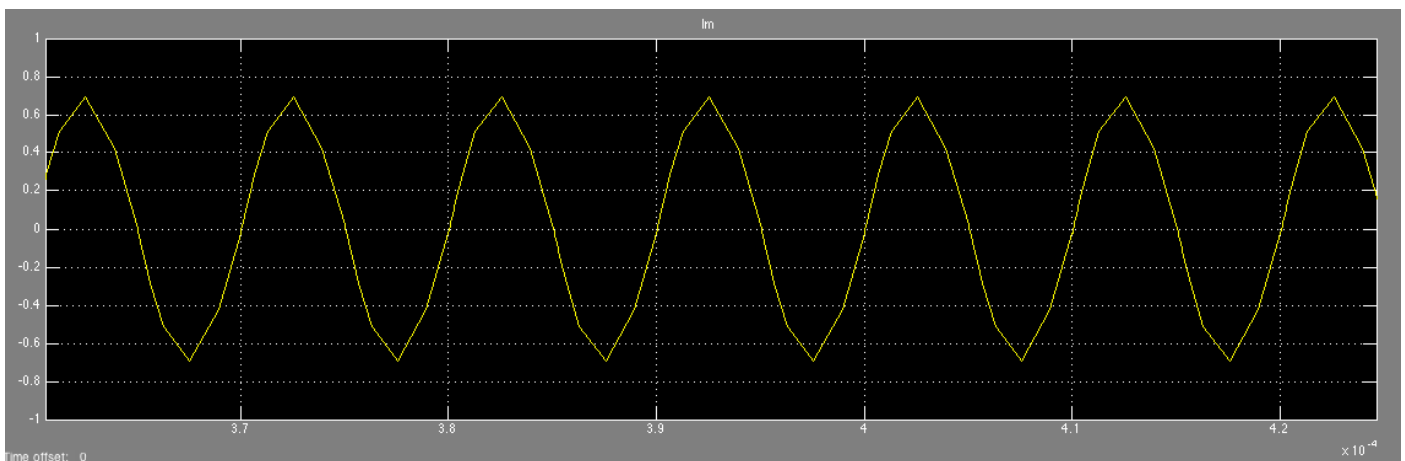e) Current and voltage waveform in resonant components I_m




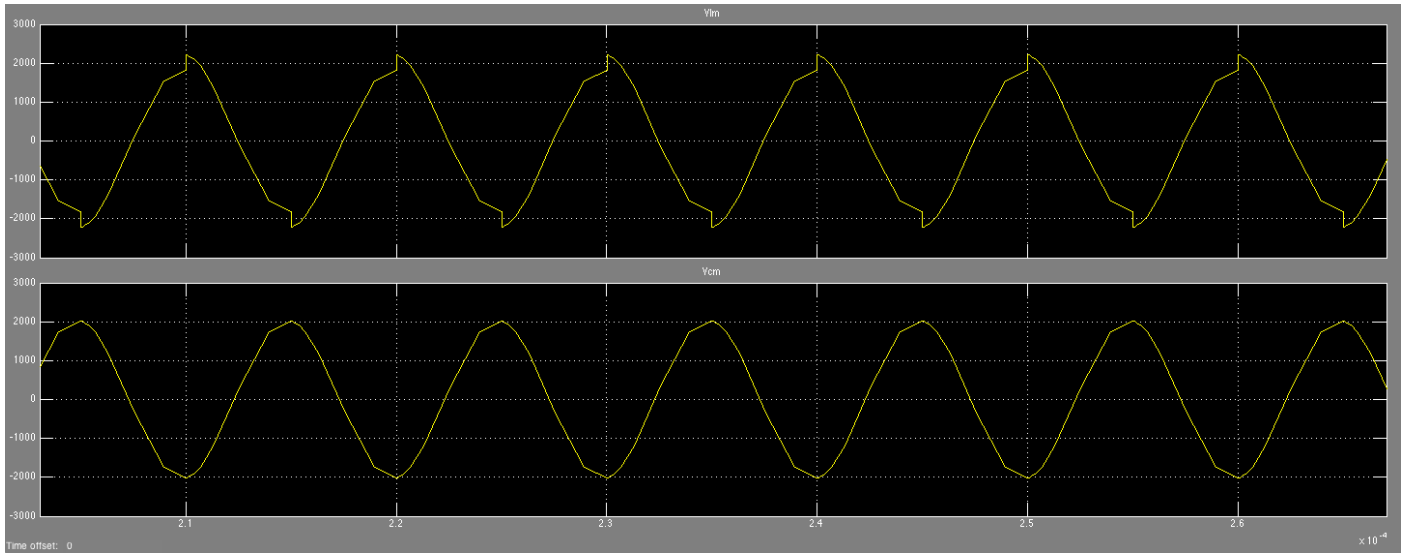f) Voltage waveform for resonant component V_{Lm} V_{Cm}




If $Q=10$, then $f_o=100.5$ kHz, $R_i=36593$ Ω , $L=5.795$ mH, $C=0.4328$ nF, $I_m=0.699$ A, $V_{Lm}=2546.48$ V, $V_{Cm}=2559.18$ V.

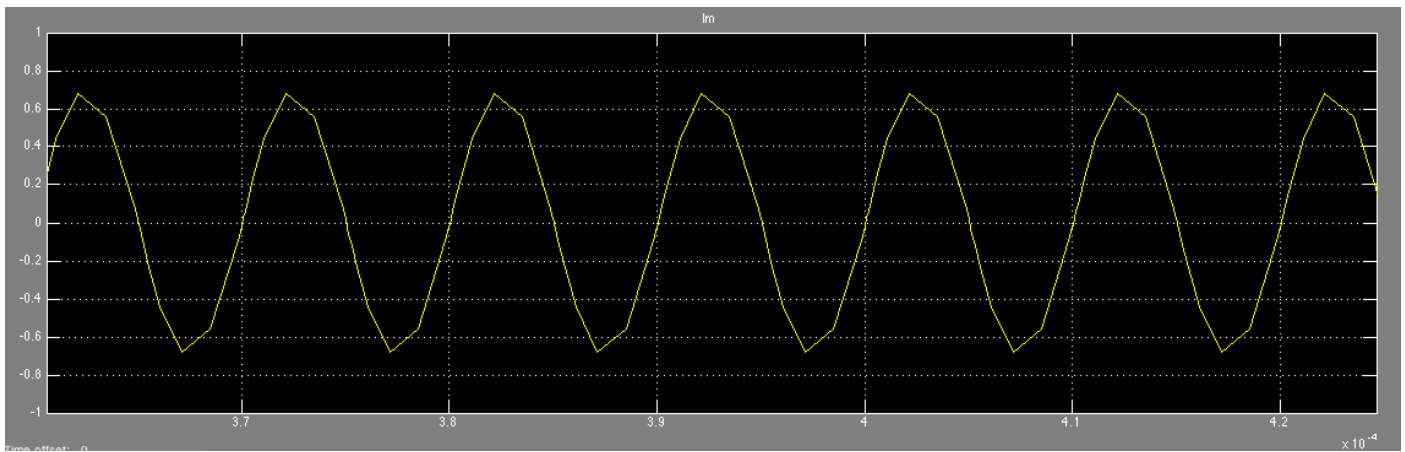g) Current and voltage waveform in resonant components I_m



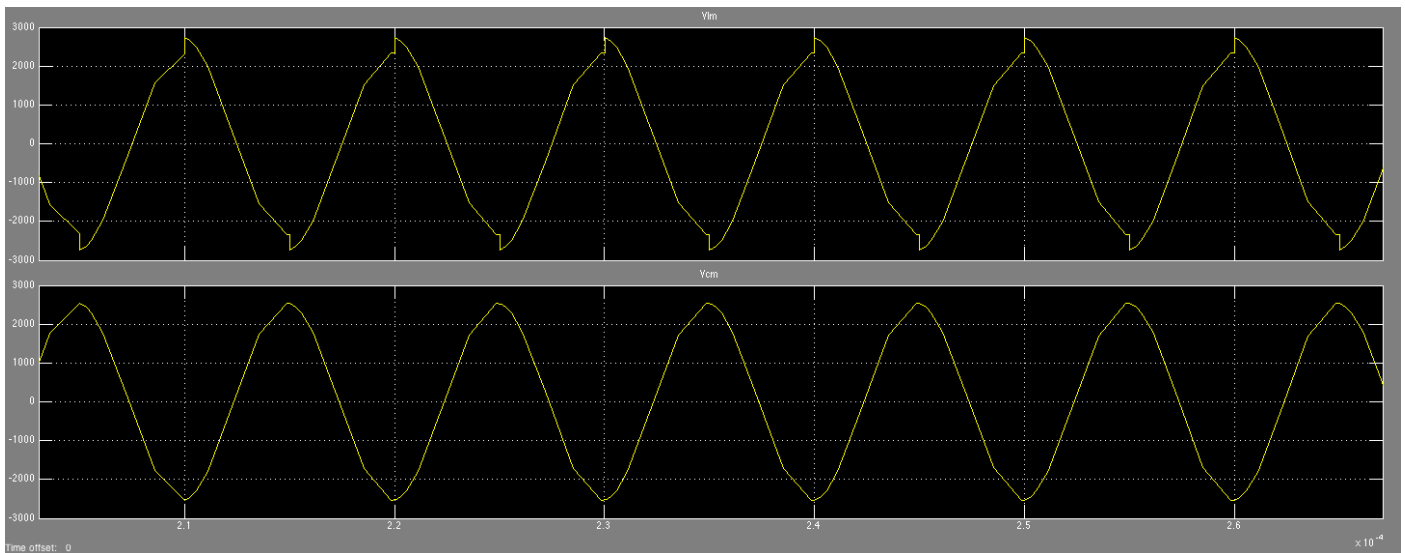h) Voltage waveform for resonant component V_{Lm} V_{Cm}



3. Show how the voltage transfer function varies with the switching frequency.

The magnitude of DC-to-AC voltage transfer function of the lossless Class D inverter is:

$$|M_{VI}| = \frac{V_{Ri}}{V_I} = \frac{2\sqrt{2}}{\pi \sqrt{\left[1 - \left(\frac{\omega}{\omega_o}\right)^2\right]^2 + \left[\frac{1}{Q_L} \left(\frac{\omega}{\omega_o}\right)\right]^2}} = \frac{2\sqrt{2}}{\pi \sqrt{\left[1 - \left(\frac{f}{f_o}\right)^2\right]^2 + \left[\frac{1}{Q_L} \left(\frac{f}{f_o}\right)\right]^2}}$$

For the lossy inverter,


$$M_{Vla} = \eta_i M_{VI}$$



The range of $|M_{VI}|$ is from 0 to ∞ .


The codes and diagrams showing transfer function $|M_{VI}|$ as a function of frequency f:

```
Q = 2.5;
f0 = 109.1;
n = 0.92;
syms f;
f = 50:0.01:150;
Mvi = 2*sqrt(2)*n/pi./sqrt((1-(f/f0).^2).^2+((f/f0)/Q).^2);
figure;
plot(f,Mvi);
xlabel('Frequency/KHz');
ylabel('Transfer function |Mvi|');
```

a. Q=2.5

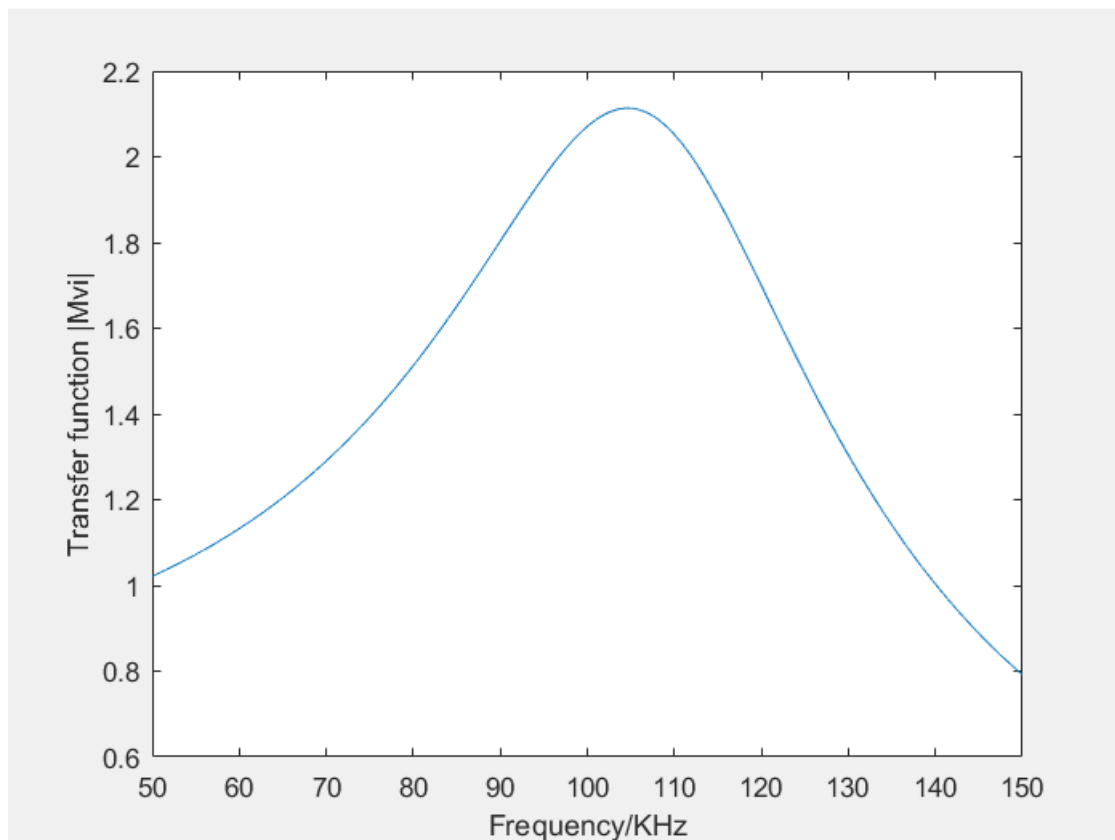

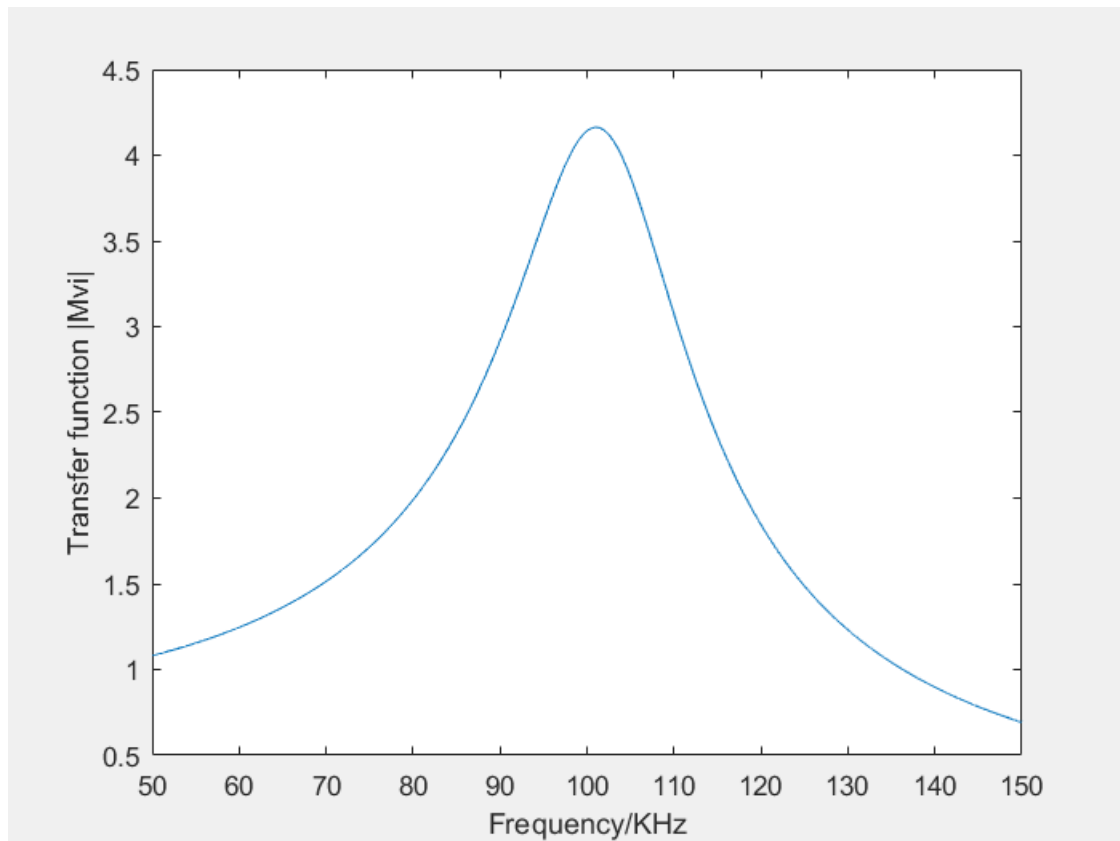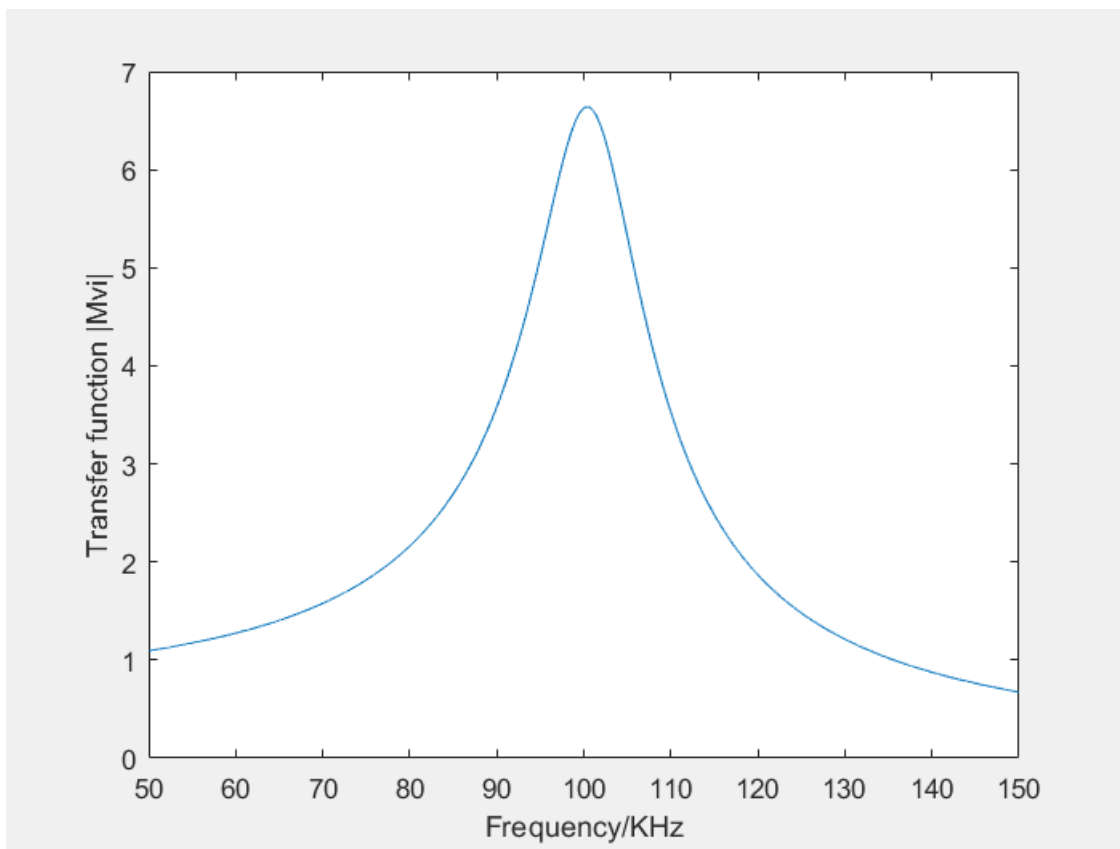b. $Q=5$ c. $Q=8$ d. $Q=10$

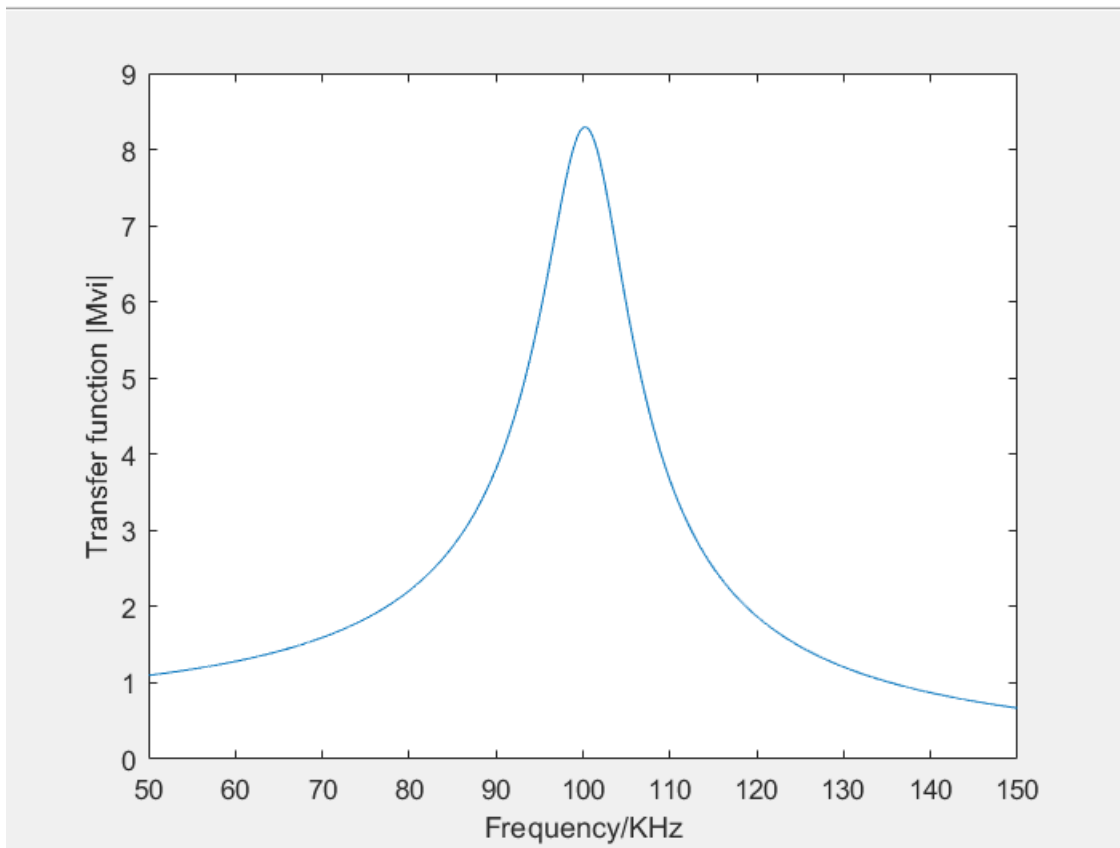

4. Conclusion

In conclusion, the transfer function changes more and more fast as the Q increases. The waveform becomes shaper and shaper. From these diagrams, we know when the value of Q increases, the values of I_m , V_{Lm} and V_{Cm} rise. Otherwise, those values reduce.